
A simple electric circuit

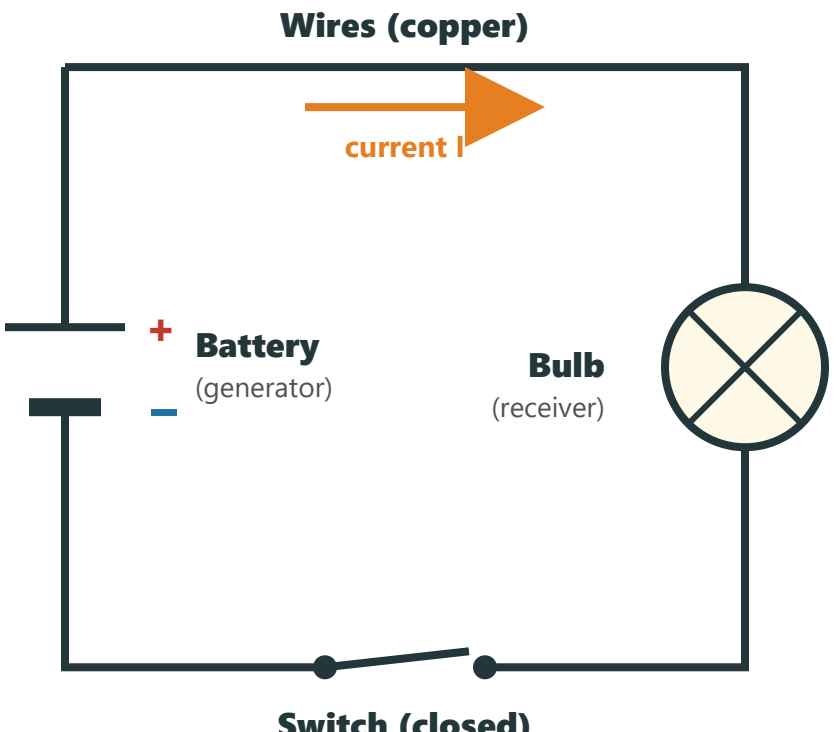

Quantity	Symbol	Unit	Measured with
Current intensity	I	ampere (A)	ammeter
Potential difference (voltage)	ΔV	volt (V)	voltmeter
Resistance	R	ohm (Ω)	ohmmeter

💧 **Water analogy**: the battery is like a pump (voltage), the current is like the flow of water, and the resistance is like a narrow pipe that makes the water flow harder.