

Series or parallel?

Series: one single path

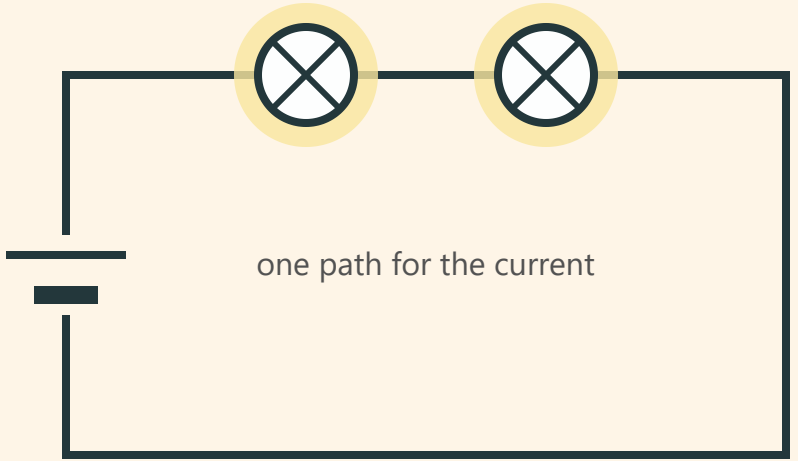

- The **same current** flows through every bulb.
- If one bulb breaks, **all** go off ✗ (old Christmas lights 🎄)

Parallel: separate branches

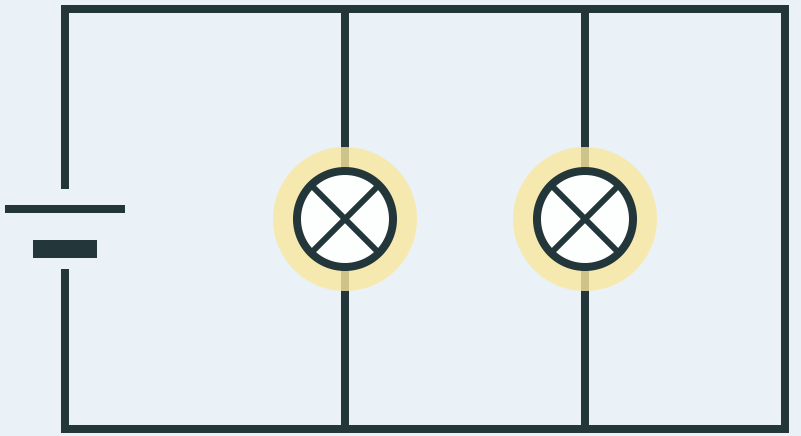

- Each branch has the **same voltage**.
- If one bulb breaks, the others **keep working** ✓ (our homes 🏠)